 


# COMP1003 Computer Organization

## Lecture 5 From Gates to Circuits I:


### Combinational Circuits



United International College
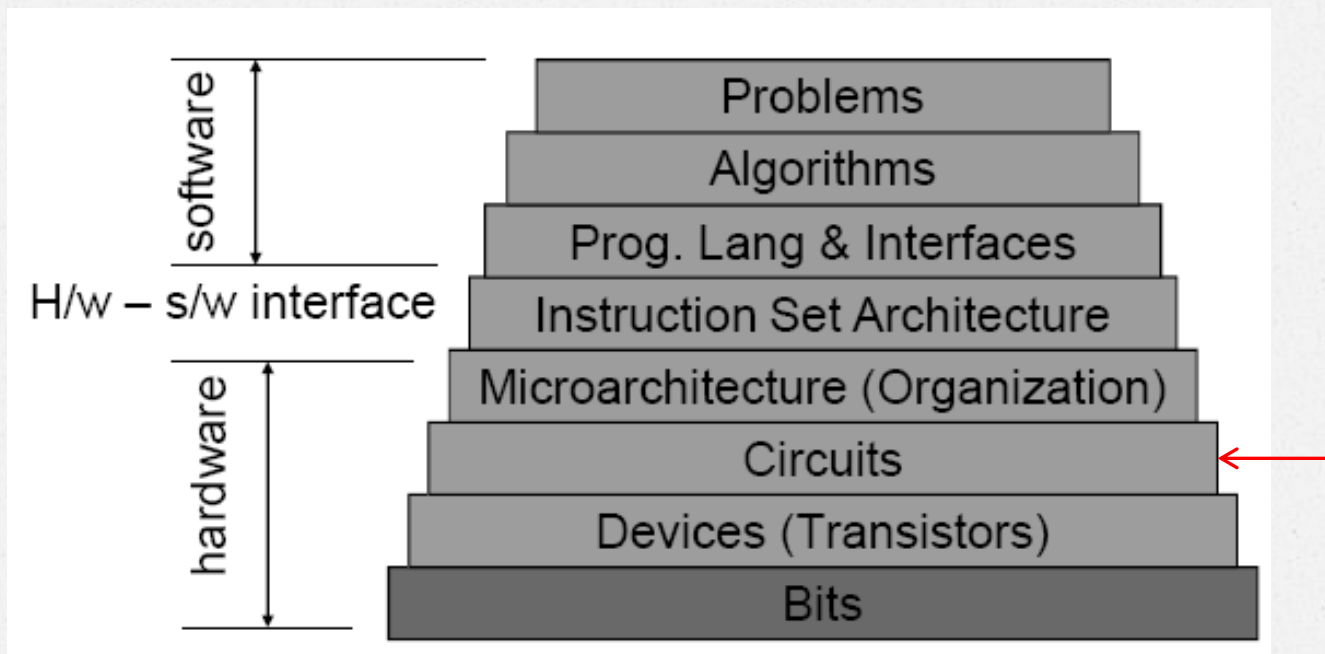
# From Gates to Circuits





- How to use logic gates to build more complex and more powerful **circuits**





    
# Basic Building Blocks

- A gate is a small, electronic device that computes various functions of two-valued signals



# Representations of Boolean Functions


- 3 representations logically equivalent to one another
  1. Truth table
  2. Logic expression
  3. Logic circuit

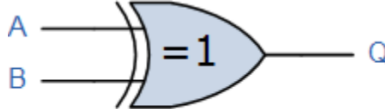Symbol	Truth Table		
 2-input Ex-OR Gate	A	B	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	0
Boolean Expression $Q = A \oplus B$			



 
# Logic Circuits

- o A collection of gates connected together to implement Boolean functions
- o Which Boolean function does the following circuit implement?


 
# Integrated Circuits (IC)

- The integration of large numbers of tiny transistors into a small chip





# Two Types of Circuits

- o Combinational logic circuits
  - o Its output depends solely on its current input.
  - o No storage, memoryless
- o Sequential logic circuits
  - o Its output depends not only on its current input, but also on its current state (previous input)
  - o Can remember previous input, storage devices

# Combinational Circuit

- o Circuit with **no memory**
- o Multiple inputs, multiple outputs, one Boolean function for each output
- o Abstracted as a package or a black box
- o Implementation described by one of
  - o n-input-, m-output-column truth table
  - o boolean function for each output variable
  - o logic diagram (possibly using other packages)




# Binary Addition

- o How to build a circuit to perform **binary addition**?
- o We start with the simplest case: adding two single bits
- o The circuit is called **half adder**
 
# Half Adder


- Only add two single bits together ( $a$ ,  $b$ ),  $s$  is the sum and  $c$  is the carry bit
- Logic Expression?
- Logic Circuit?



$a_i$	$b_i$	$c_{i+1}$	$s_i$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0




# Half Adder Circuit

 
 
# Full Adder


- Add 3 bits together (A, B, Carry-in)
- Logic expression?
- Logic circuits?



$A_i$	$B_i$	$C_i$	$C_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1





# Full Adder Diagram

 
  
# 4-bit Adder

- Full adder only adds three bits together
- But we can build an adder capable of adding two 4-bit words by replicating the above circuit 4 times
  - feeding the Carry Out of one circuit into the Carry In of the circuit immediately to its left
- This is called a “ripple-carry adder” (very slow!)







# Decoder

- o A **decoder** uses the inputs and their respective values to **select one specific output line**.
  - o – from a set of **n inputs** to a maximum of  **$2^n$  outputs**
  - o – for a given input, **one unique output line is asserted**, or set to 1, while the other output lines are set to zero
- o All **memory addresses** in a computer are specified as binary numbers.
  - o When a memory address is referenced (whether for reading or for writing), the computer first has to determine the actual address.
  - o This is done using a decoder

# A 2-4 Decoder

 

E	$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

 


What are the logic expressions?




 
# Multiplexer

- A multiplexer behaves like a **channel selector**
- It **selects a single output from several inputs.**
- The particular input chosen for output is determined by the value of the multiplexer's **control lines.**
- To be able to select among **n** inputs,  $\log_2 n$  control lines are needed



# 4-to-1 Multiplexer

What are the logic expressions?

  


$E$	$S_1$	$S_0$	$Y$
1	0	0	$I_0$
1	0	1	$I_1$
1	1	0	$I_2$
1	1	1	$I_3$
0	x	x	0



 
# Combinational Circuit Analysis

- find the logic function that the following circuit implement




# 1-bit ALU

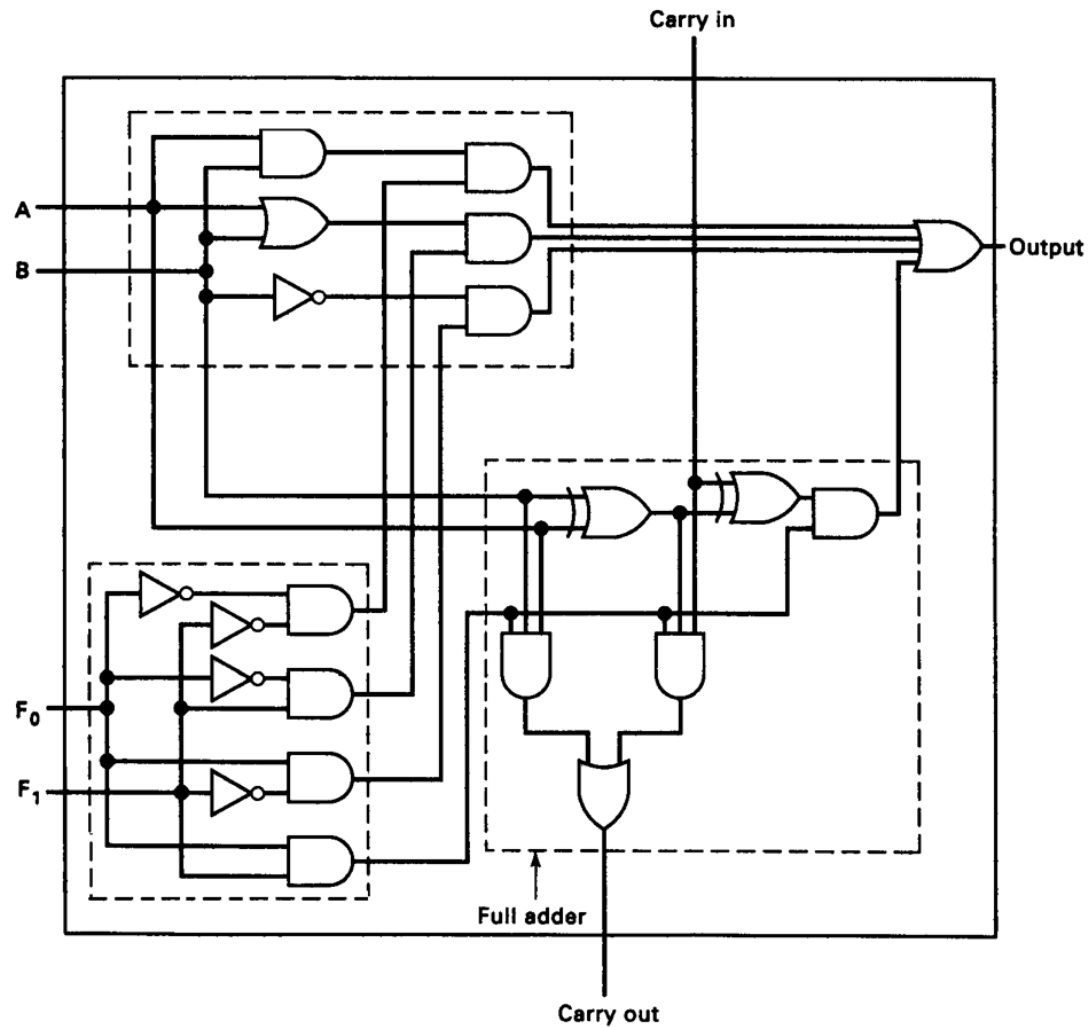



# 2-bit ALU

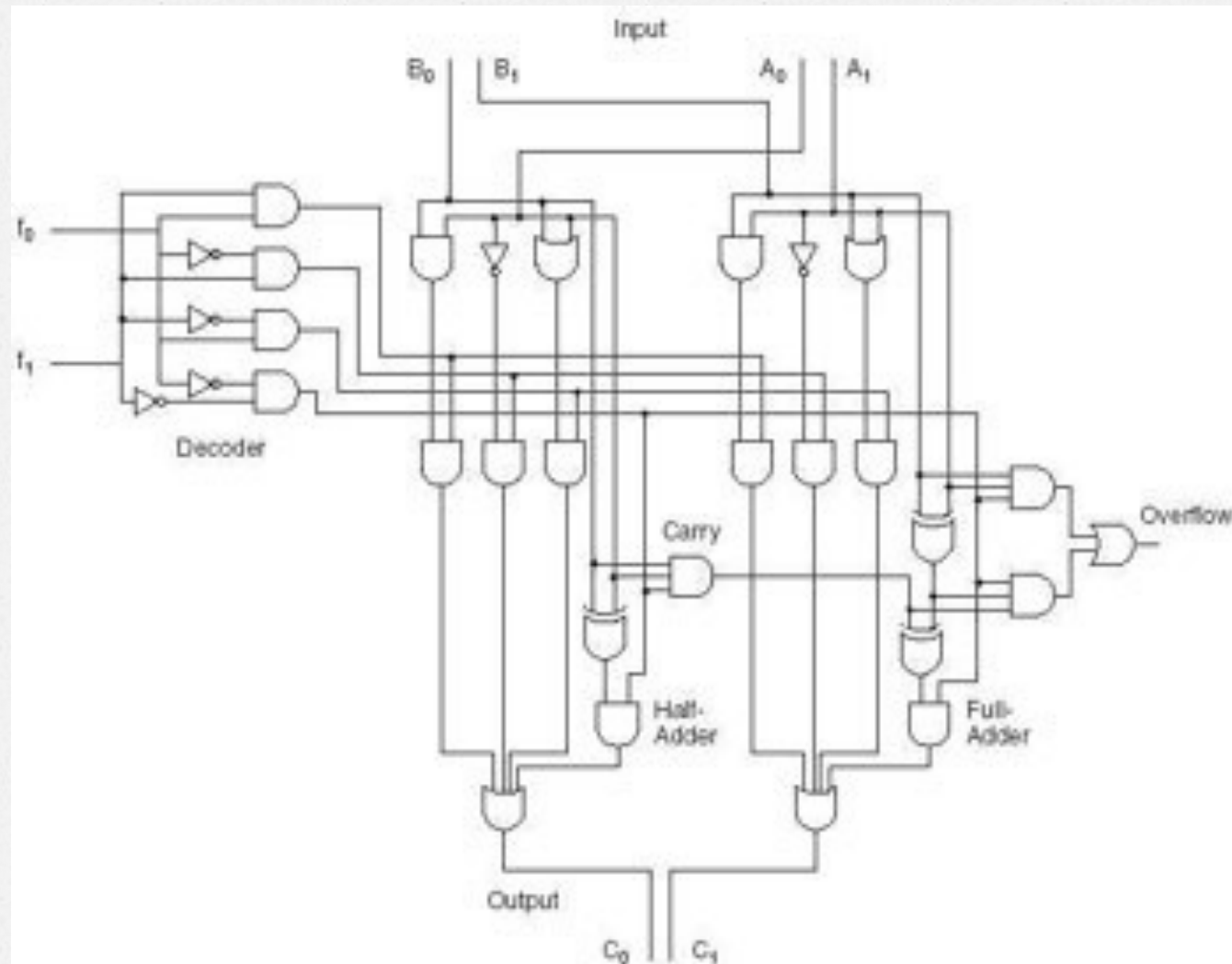

# Combination Circuit Design

1. From the design specification, obtain the **truth table**
2. From the truth table, derive the **Sum of Products Boolean Expression**.
3. Use Karnaugh Map to **minimize the Boolean expression**.
4. Use logic gates to **implement the simplified Boolean Expression**.
5. Verify the result.



# Combination Circuit Design

- o design a circuit that compares 1-bit number, A and B. The circuit should have
- o three outputs:
  - o – G (“Greater”) should be 1 only when  $A > B$
  - o – E (“Equal”) should be 1 only when  $A = B$
  - o – L (“Lesser”) should be 1 only when  $A < B$

# Truth Table

How many inputs?

How many outputs?

Fill in the truth table

Inputs		Outputs		
B	A	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0



# Derive the Logical Expression

- Write the logical expression for each output in canonical forms (SOP or POS)
- Simplify the logical expression


$$C = \bar{A}B \longrightarrow A < B$$

$$D = \overline{\bar{A}B + A\bar{B}} \longrightarrow A = B$$

$$E = A\bar{B} \longrightarrow A > B$$

Inputs		Outputs		
B	A	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

# Draw the Logical Diagram

 



# Summary

- Combinational Circuit
  - No memory
  - Basic building blocks
  - Abstracted as package
- Examples
  - Half adder
  - Full adder
  - Decoder
  - Multiplexer
  - ALU
- Combinational Circuit Analysis & Design