

Computer Organization

Lab4

Group9



Contents

01

Design Target

02

Design Process

03

Design Truth Table






01

Design Target



Design Target

 - Design a **4-bit binary counter system**
- Displays numbers ranging from 00 to 15



- Using **two seven-segment displays**

The background features abstract, organic shapes in dark blue and light blue, with thin orange lines and small circles scattered throughout. The text is centered on a white background.


02

Design Progress



Key System Components — 4-bit binary counter

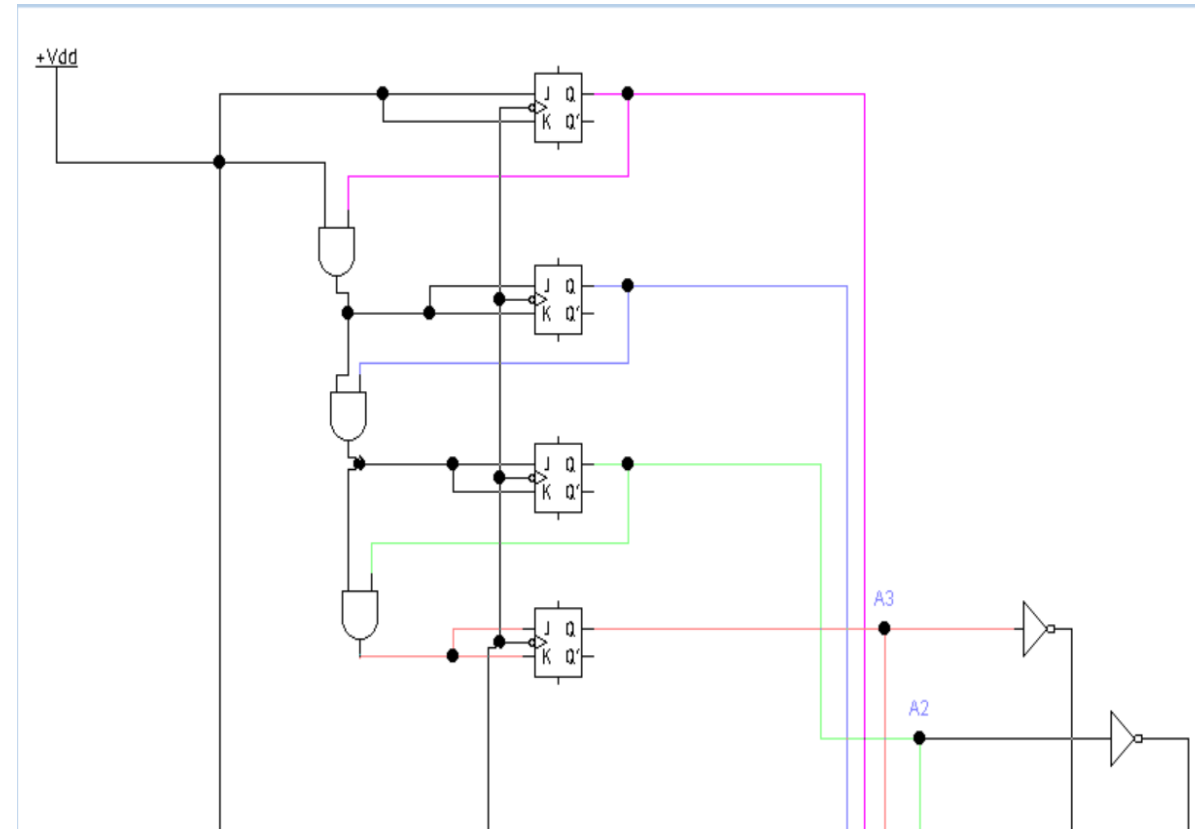- ❑ Composed of four JK flip-flops.
- ❑ Generates a 4-bit binary output (A3, A2, A1, A0), representing numbers from 0 to 15.





Design Progress——Key Components

Key System Components —— 7-segment display

- Units Display:


Displays values from 0 to 9 to represent the units digit of the counter value.

Driven by decoded signals (S_a , S_b , S_c , S_d , S_e , S_f , S_g) generated from the 4-bit counter output (A_3 , A_2 , A_1 , A_0).

- Tens Display:

Displays values of 0 or 1 to represent the tens digit of the counter value.

 Controlled by signal N , indicating whether the current value exceeds 9.






Key System Components —— clock

we connect the output of the clock to the clock input of the counter. The counter will increase by 1 at every clock cycle.

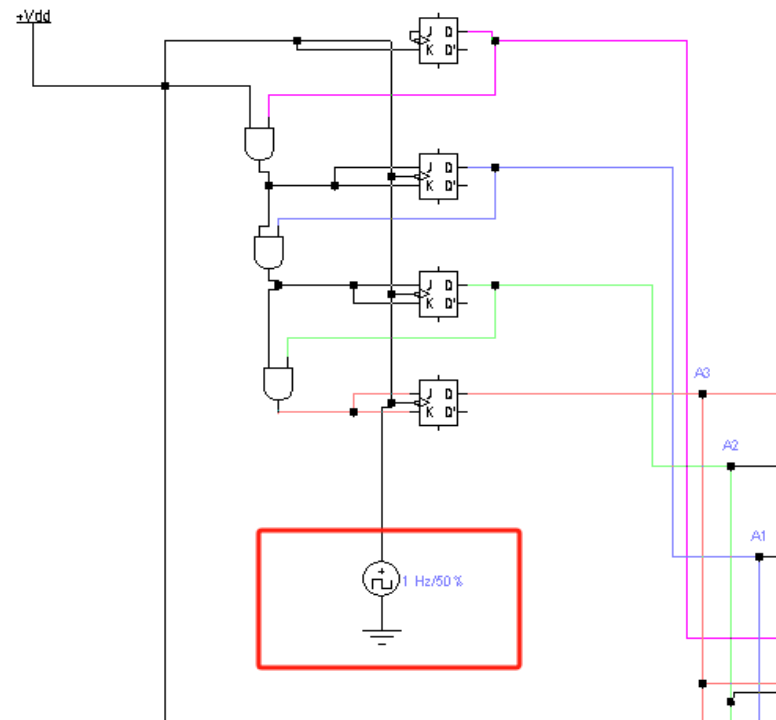We set the clock in “1Hz/50%”, which means the frequency is 1 time/s and the duty cycle is 50%





Design Progress——Truth Table


A3	A2	A1	A0	Sa	Sb	Sc	Sd	Se	Sf	Sg	N
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	1	0	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1	0
0	0	1	1	1	1	1	1	0	0	1	0
0	1	0	0	0	1	1	0	0	1	1	0
0	1	0	1	1	0	1	1	0	1	1	0
0	1	1	0	1	0	1	1	1	1	1	0
0	1	1	1	1	0	1	1	1	1	1	0
1	0	0	0	1	1	1	0	0	0	0	0
1	0	0	1	1	1	1	1	1	1	1	0
1	0	1	0	1	1	1	1	0	0	1	0
1	0	1	1	0	1	1	0	0	0	0	1
1	1	0	0	1	1	0	1	1	0	1	1
1	1	0	1	1	1	1	1	0	0	1	1
1	1	1	0	0	1	1	0	0	1	1	1
1	1	1	1	1	0	1	1	0	1	1	1



Design Progress——K-Map

输出:

格式:

 

$$\overline{A2} \overline{A0} + \overline{A3} A1 + A2 A0 + A3 \overline{A1}$$

设为表达式

输出:

格式:




$$\overline{A2} + \overline{A1} \overline{A0} + \overline{A3} A1 A0 + A3 \overline{A1} + A3 \overline{A0}$$

设为表达式

输出:

格式:

 


$$\overline{A3} \overline{A1} + \overline{A0} + A2 A1 + A3 \overline{A2}$$

设为表达式

输出:

格式:

 


$$\overline{A2} \overline{A0} + \overline{A3} \overline{A2} A1 + \overline{A3} A1 \overline{A0} + A2 \overline{A1} A0 + A3 \overline{A1} \overline{A0} + A3 A2 A0$$

设为表达式

输出:

格式:

 


$$\overline{A2} \overline{A0} + \overline{A3} A1 \overline{A0} + A3 \overline{A1} \overline{A0}$$

设为表达式

输出:

格式:

 


$$\overline{A3} \overline{A1} \overline{A0} + \overline{A3} A2 \overline{A1} + \overline{A3} A2 \overline{A0} + \overline{A3} A2 A1 + A3 \overline{A2} \overline{A0} + A3 A2 A1$$

设为表达式

输出:

格式:

 


$$\overline{A3} \overline{A2} A1 + A2 \overline{A1} + A2 \overline{A0} + A3 \overline{A1} + A3 A2$$

设为表达式

输出:

格式:

 

$$A3 A1 + A3 A2$$

设为表达式



Design Progress— Truth Table

N	Sa	Sb	Sc	Sd	Se	Sf	Sg
0	1	1	1	1	1	1	0
1	0	1	1	0	0	0	0



Thank you